

ROBO
DYNAMICS

*Build
Your Own
Robot*

**Project 2: Fun with
Electronics**

Session Objective

- **In this project, we are going to see how a light bulb works with a switch, like the one in our homes?**

Do you also have these Questions ???



How do you think
a light bulb
works with a
switch, like the
one in our homes?



We also do !!!!

Project 2

LED with a Switch

A yellow speech bubble with a jagged, starburst-like border, containing the word "Wow!" in a stylized, pink, handwritten font.

Wow!


LED with Battery !!!



Components Needed



9V Battery

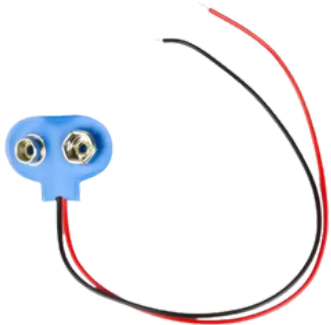

Battery Connector



Breadboard



Switch




LED

Project : LED with Battery !!!



Step 1

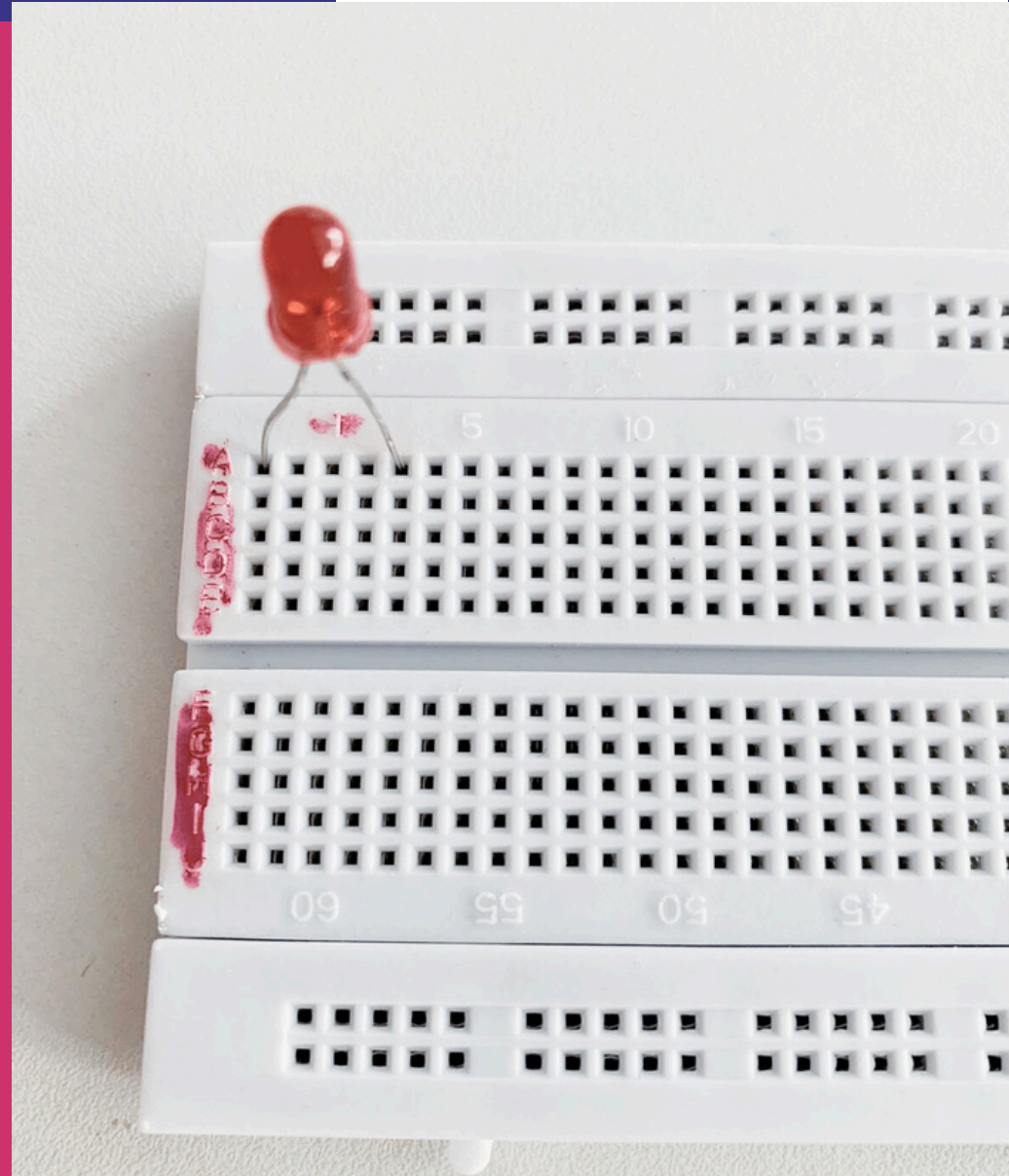- Take a Breadboard
- Take a Led, and you see two terminals popping out, a longer one and a shorter one now insert the longer one in the first row(A1)




Project : LED with Battery !!!



Step 2

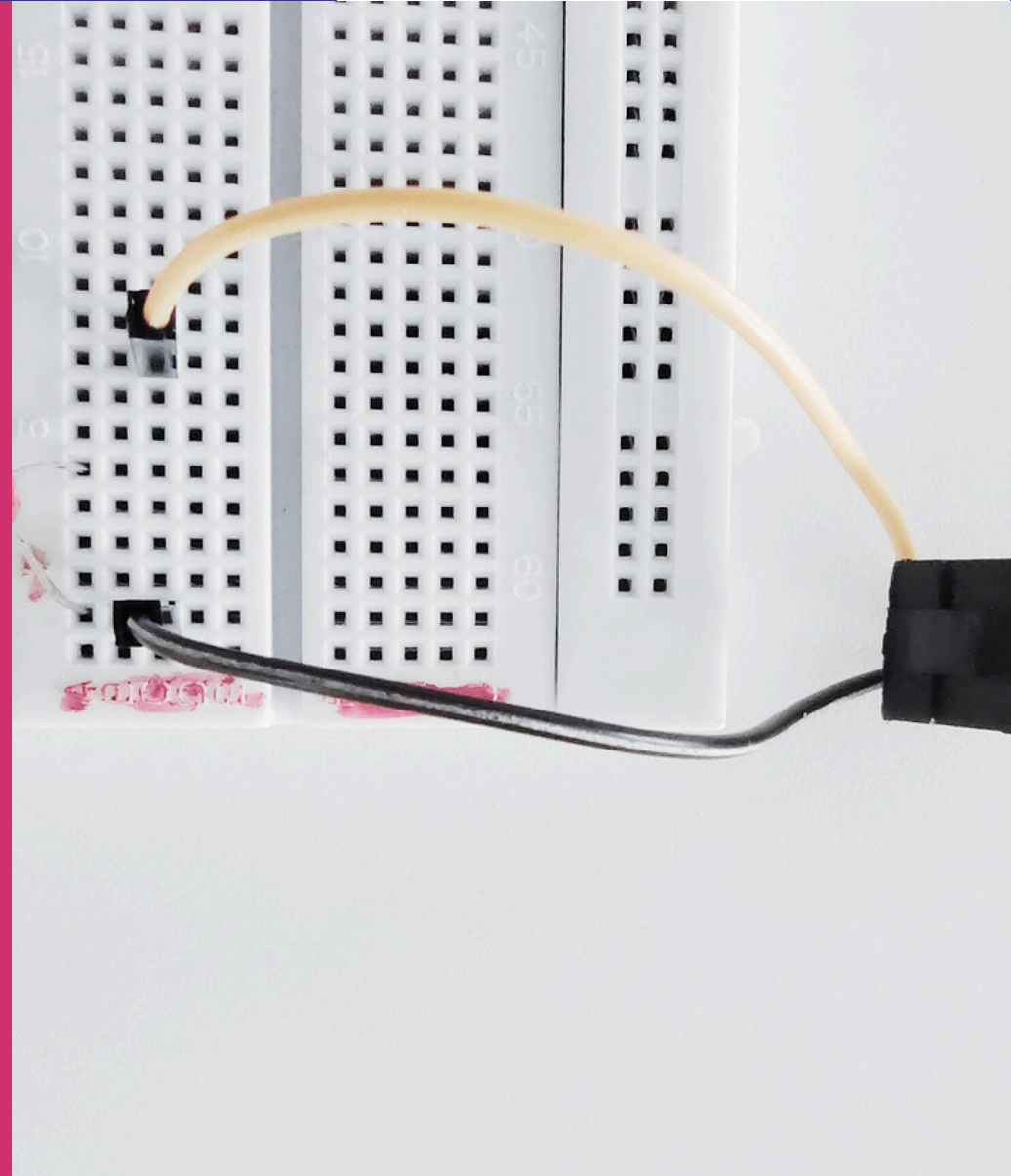- Take a resistor, connect one in the same column as the longer terminal of led(C1) and the other towards left




Project : LED with Battery !!!




Step 3

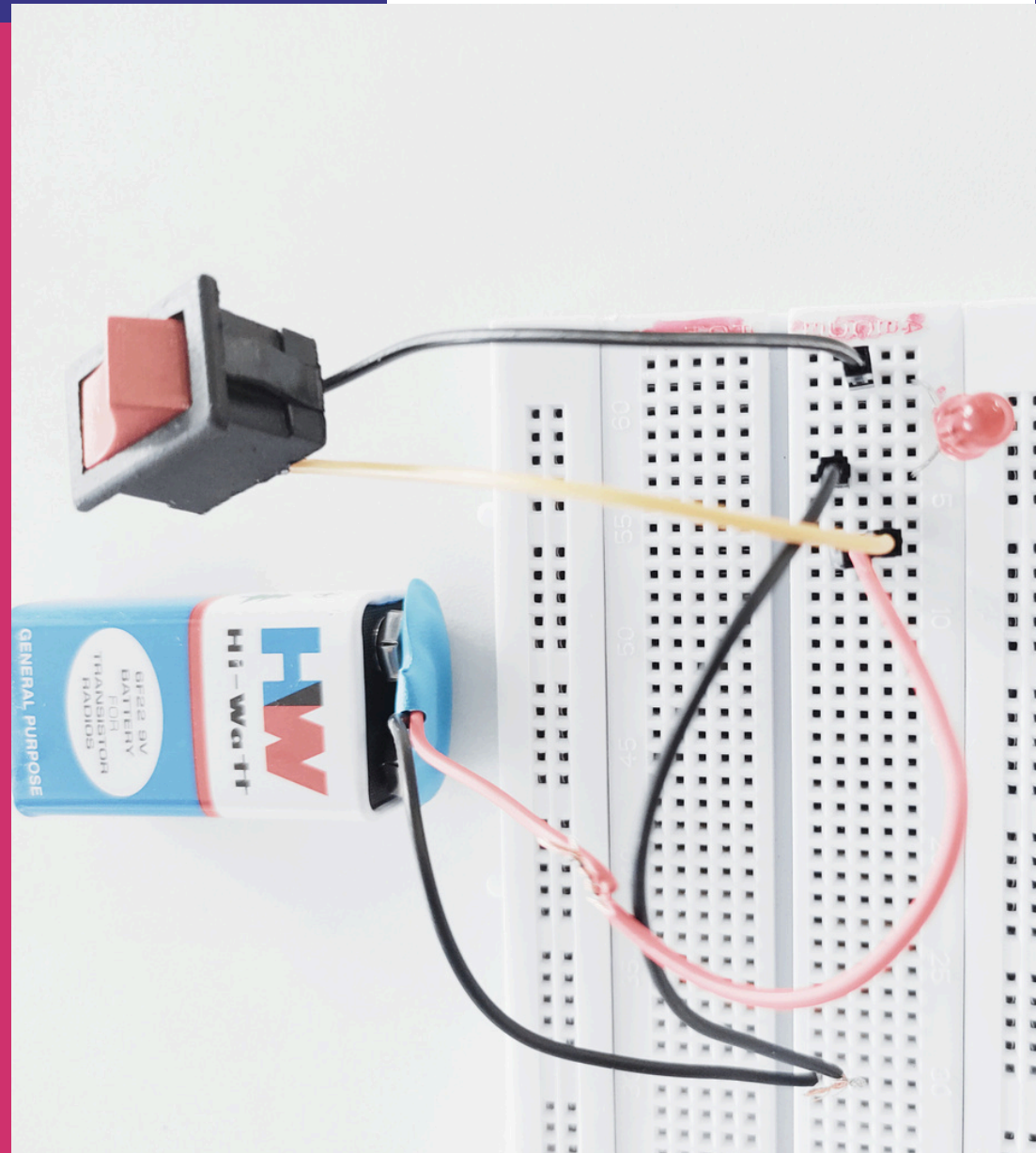- Take a resistor, connect one in the same column as the longer terminal of led(C1) and the other towards left



Project : LED with Battery !!!

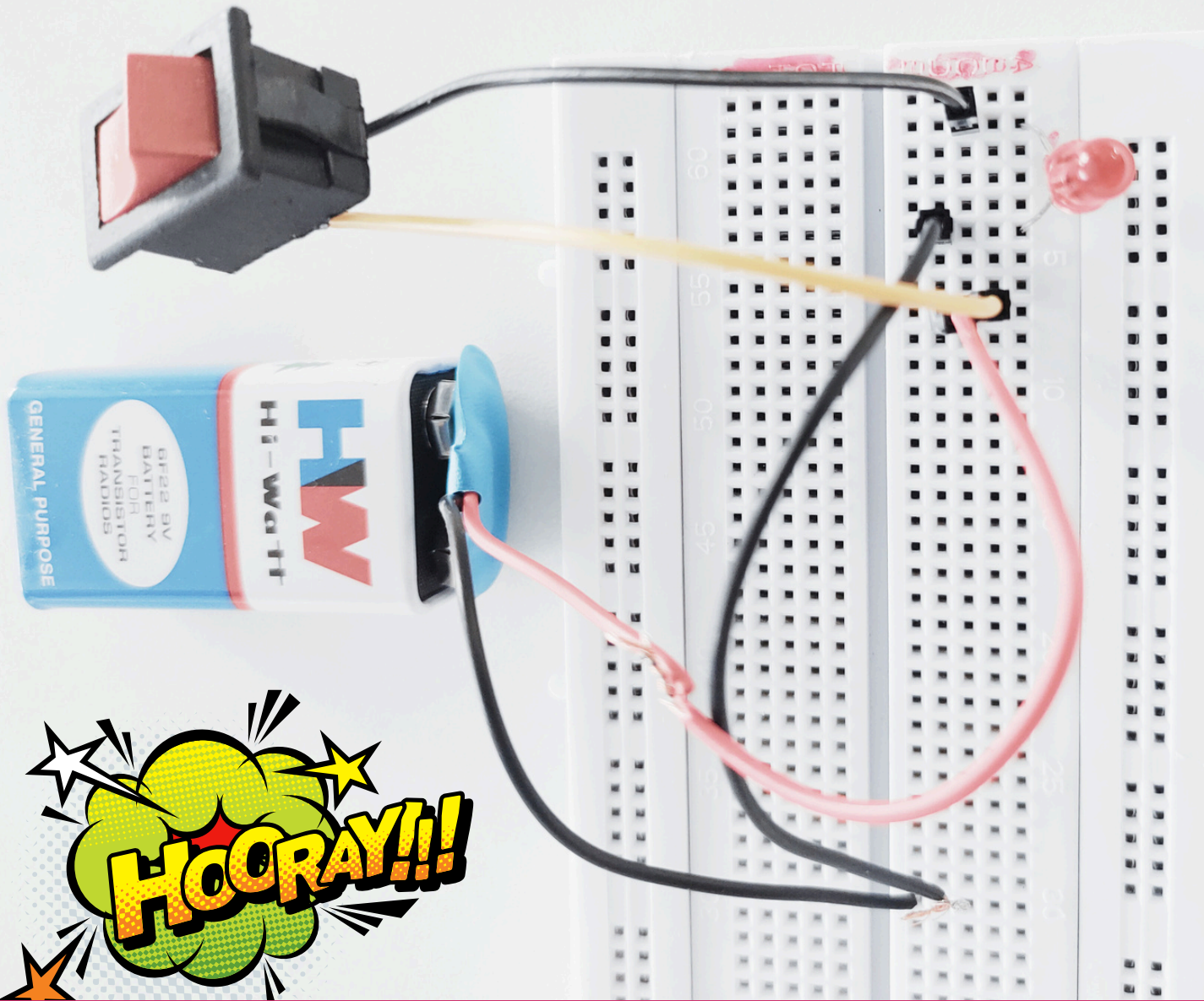

Final
Output

Do You
See LED
Glowing with a
switch?




Project : LED with Battery !!!



AWESOME



AWESOME

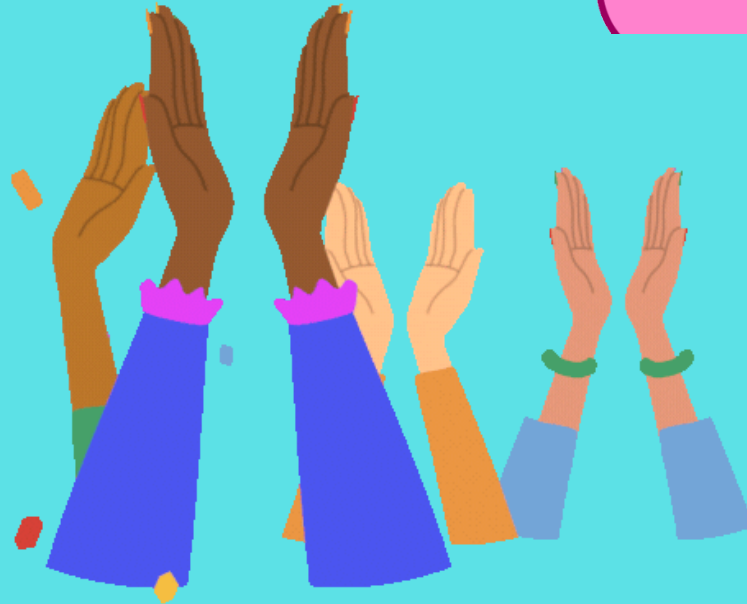

Project : LED with Battery !!!



TRY ON

YOUR OWN

!!!

Project : LED with Battery !!!

